



### SECTION-B

- 2) a) A series circuit consists of a  $115\Omega$  resistor, a  $0.024\ \mu\text{F}$  capacitor and coil of inductance  $L$ . If the resonant frequency of the circuit is  $1000\ \text{Hz}$ , determine Inductance and bandwidth.  
  
b) Compare electric and magnetic circuits. Establish the relationship between magnetomotive force, magnetic flux and magnetic reluctance.
- 3) Draw & explain the phasor diagram of RLC series circuits and give the condition for resonance in this circuit.
- 4) Explain the working principle & construction of three phase induction motor.
- 5) Explain the construction & working of induction type energy meter.

### SECTION-C

- 6) What is LVDT? Explain its use for the measurement of displacement.
- 7) What is Zener Diode? Explain its use as voltage regulator.
- 8) a) What are the different logic gates? Give their truth tables.  
  
b) Discuss the working of a full wave rectifier.
- 9) Draw the equivalent circuit & truth table of RS Flip-Flop.

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**